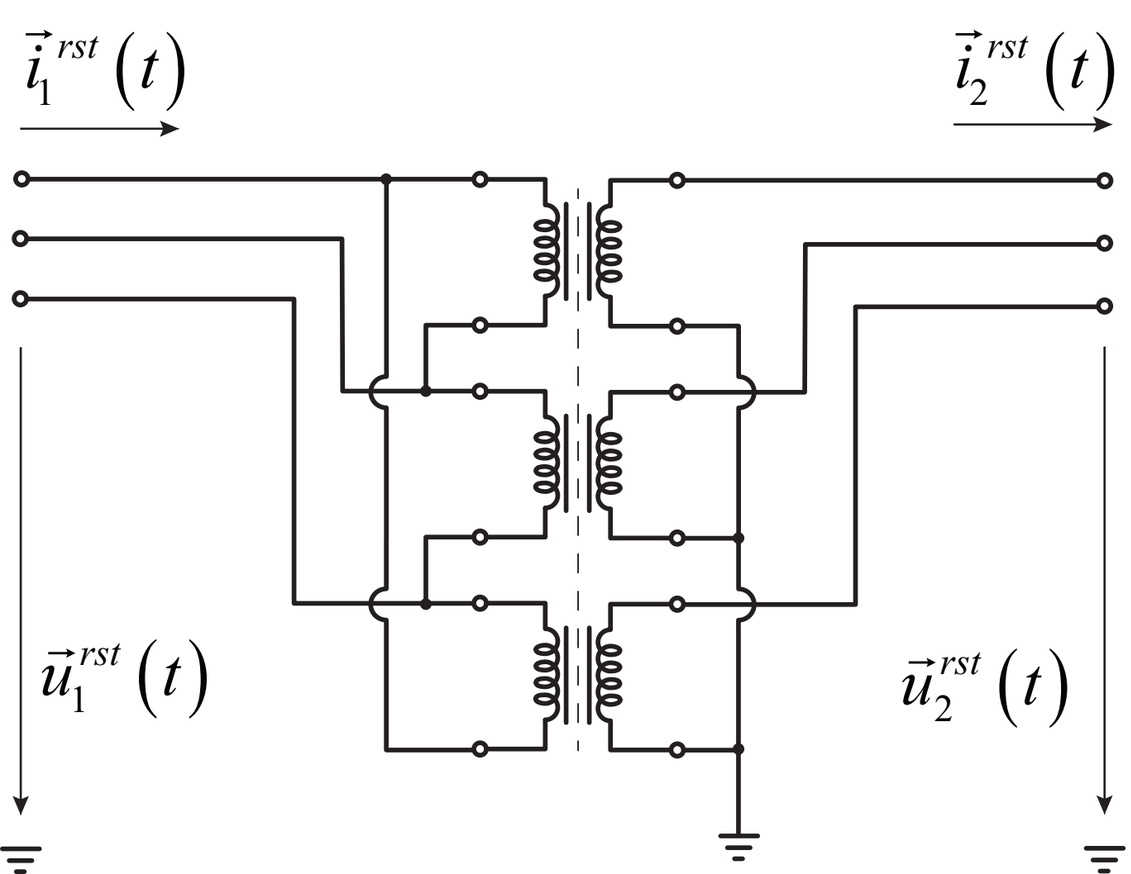

Per-phase equivalent circuit

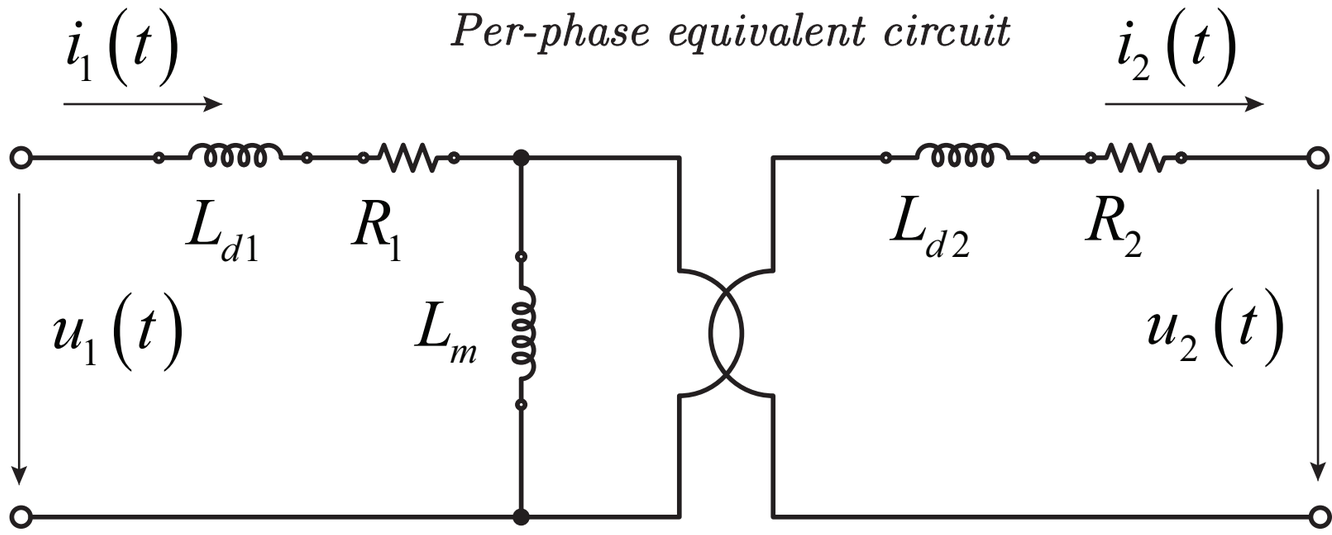

$$L_\sigma = L_{d1} + L_{d2}$$